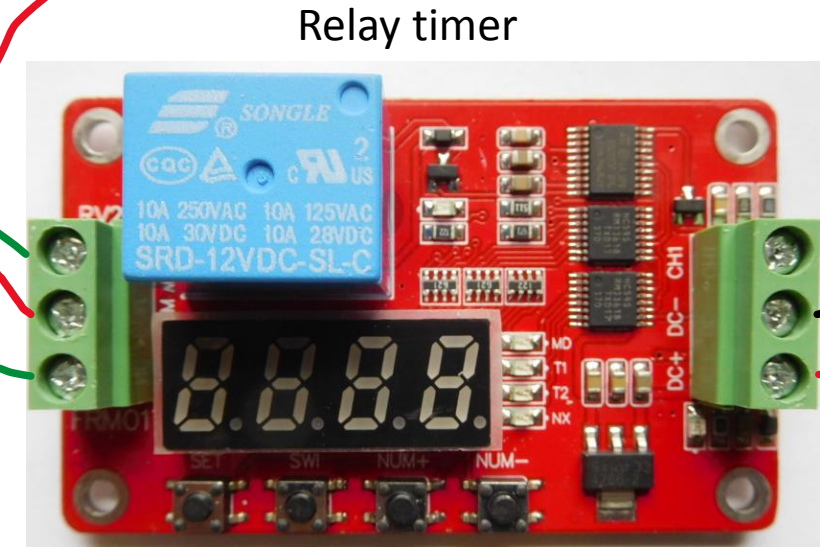





Lionel 154



Relay timer

AC control

DC in

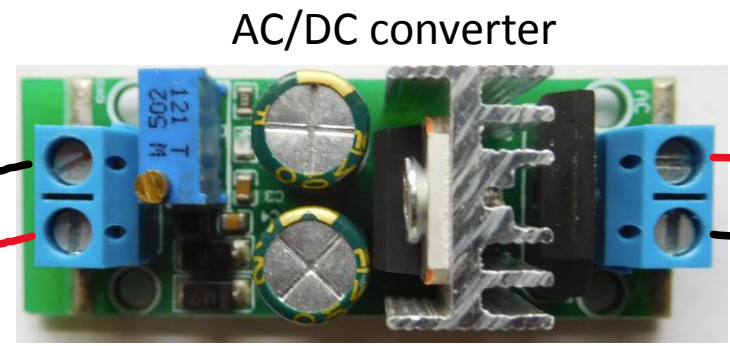

AC/DC converter

DC out

AC in

To AC 14 volts from transformer

Flashing
highway
signal



Insulated rail



Block Signal Control

To transformer common

To AC 14 volts from transformer

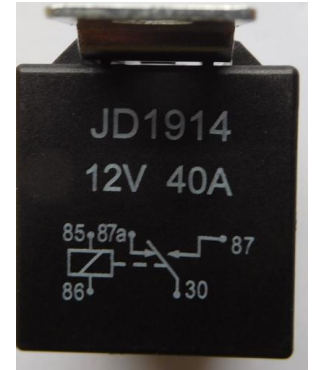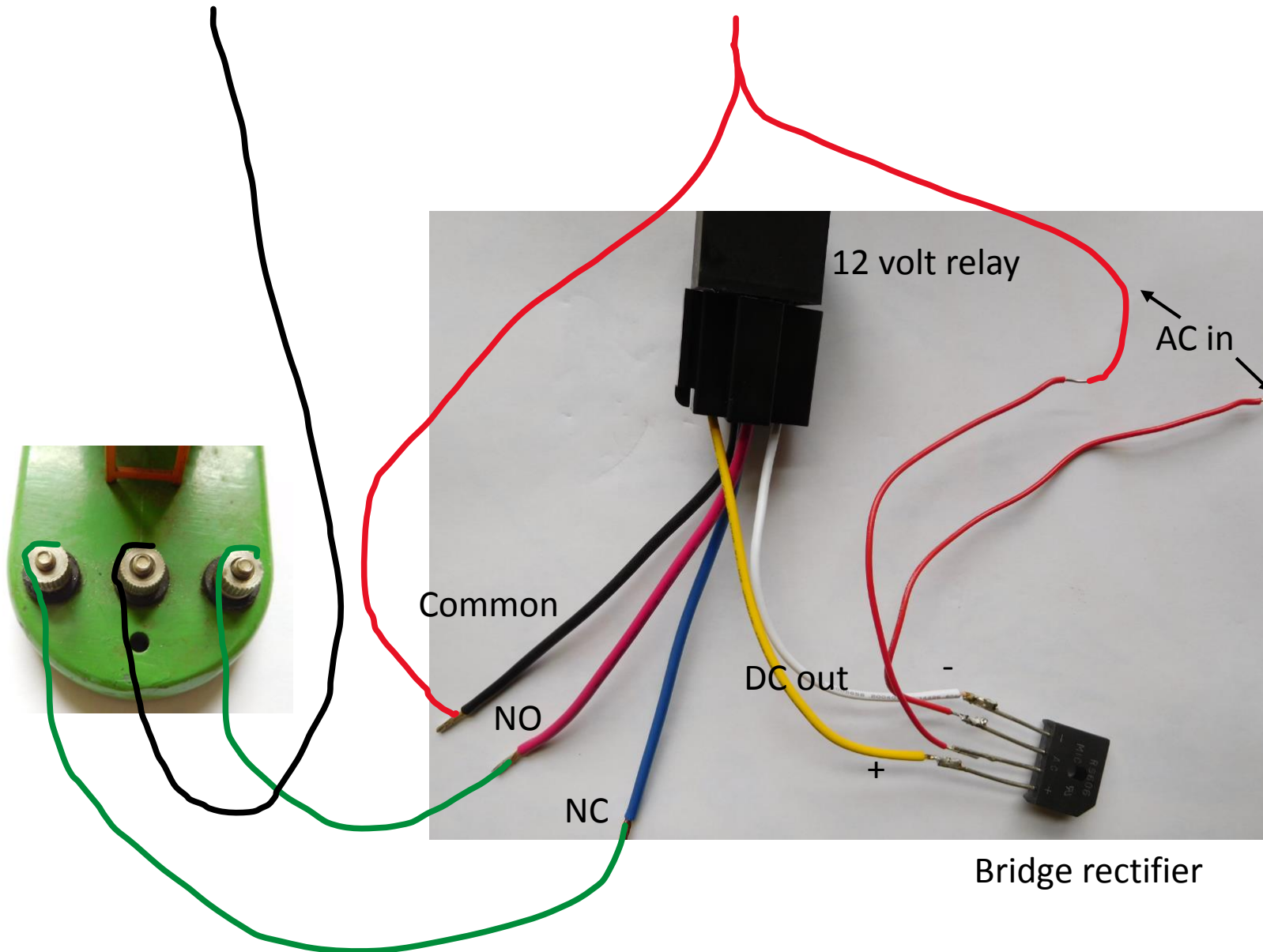

12 volt relay



Insulated rail



Lionel 153